

SRK/KW/14/6934/6939

Faculty of Engineering & Technology
Third Semester B.E. (Electronic/ET/EC) (C.B.S.)
Examination
NETWORK ANALYSIS AND SYNTHESIS

Time—Three Hours]

[Maximum Marks—80

INSTRUCTIONS TO CANDIDATES

- (1) All questions carry marks as indicated.
 - (2) Due credit will be given to neatness and adequate dimensions.
 - (3) Assume suitable data wherever necessary.
 - (4) Illustrate your answers wherever necessary with the help of neat sketches.
 - (5) Use of Slide rule, Logarithmic tables and non-programmable calculator is permitted.
1. (a) For the network shown in Fig. 1(a), find the current through $100\ \Omega$ resistance due to d.c. sources. Also

find the current through inductor under steady-state.

5

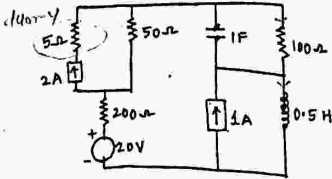


Fig. 1(a)

(b) Write the mesh basis equilibrium equations in matrix form for the network shown in Fig. 1(b).

8

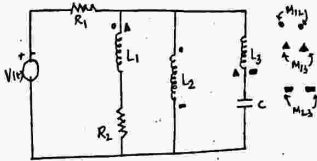


Fig. 1(b)

OR

2. (a) Explain the term duality. Find the dual of the network shown in Fig. 2(a).

6

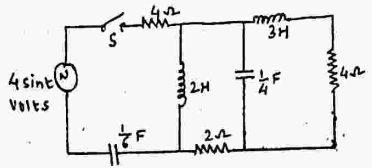


Fig. 2(a)

(b) Determine the node voltages V_A and V_B and find out power dissipated in the resistance of 3Ω in the circuit shown in Fig. 2(b) using nodal analysis.

7

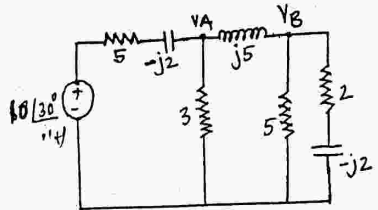


Fig. 2(b)

3. (a) Determine voltage V of Fig. 3(a) such that the current through the impedance $(3 + j4) \Omega$ is zero. Use Thevenin's theorem. 7

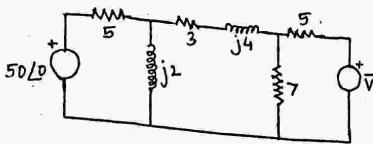


Fig. 3(a)

- (b) In the network shown in Fig. 3(b) find 'I' and verify reciprocity theorem. 7

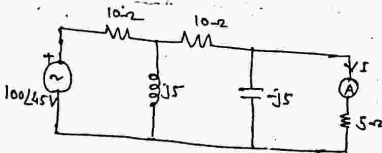


Fig. 3(b)

OR

4. (a) Find the impedance to be connected across terminals

- A and B of Fig. 4(a) for maximum power transfer. Find also the value of P_{max} . 7

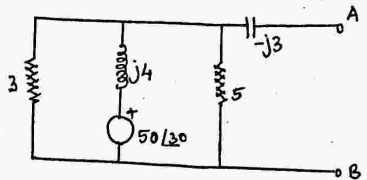


Fig. 4(a)

- (b) State the Superposition theorem. Find current through 5Ω resistance by superposition theorem shown in Fig. 4(b). 7

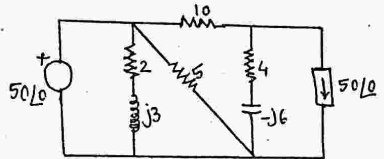


Fig. 4(b)

5. (a) Explain resonance in series R-L-C circuit in detail. Also derive the expression for resonant frequency. 6

(b) A series R-L-C circuit consists of $R = 1000 \Omega$, $L = 100 \text{ mH}$ and $C = 10 \mu\text{F}$. The applied voltage across the circuit is 100 V :

- (i) Find the resonant frequency of the circuit.
- (ii) Find the quality factor of the circuit at resonant frequency.
- (iii) Calculate half power frequencies.
- (iv) Calculate the bandwidth of the circuit. 7

OR

6. (a) Derive an expression for resonant frequency of the parallel circuit shown in Figure 6(a). 6

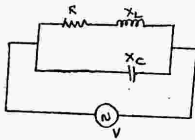


Fig. 6(a)

(b) A coil of resistance 20Ω and inductance $200 \mu\text{H}$ is in parallel with a variable capacitor. The voltage of the supply is 200 V at a frequency of 10^6 Hz . Calculate :

- (i) The value of capacitor to give resonance.
- (ii) The Q factor of the coil.
- (iii) The current in each branch of the circuit at resonance. 7

7. (a) Design a prototype band pass filter section having cut-off frequencies of 2000 Hz and 5000 Hz with nominal characteristic impedance of 600Ω . 6

(b) Design m-derived low pass filter terminated by 600Ω resistance and cut-off frequency of 1000 Hz and frequency of infinite attenuation of 1250 Hz . Show both T and π -sections. 7

OR

8. (a) Explain the design of T type attenuator. 6

(b) Design a balanced and symmetrical π type attenuator to give 15 decibal loss. The characteristic impedance

of the attenuator is 600Ω . Draw the network designed and derive the equations used. 7

9. (a) Write the equation for following voltage waveform and find its Laplace transform. Refer Fig. 9(a). 6

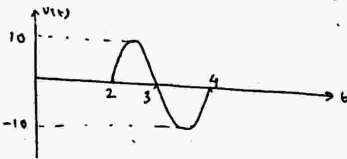


Fig. 9(a)

- (b) Find current $i(t)$ in the Fig. 9(b) if the switch is in position 'A' till steady state is reached and is shifted to 'B' at $t = 0$. Use Laplace transform. 7

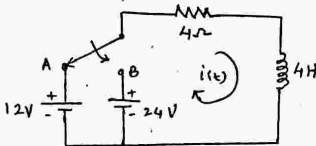


Fig. 9(b)

OR

10. (a) In the network shown in Fig. 10(a) switch K is in position 'a' for a long time. At time $t = 0$, K is moved to position 'b'. Find voltage $V_2(t)$ for $t > 0$. 6

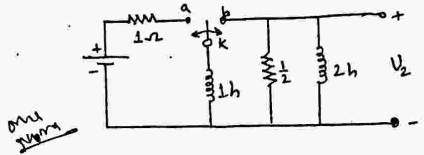


Fig. 10(a)

- (b) In the Fig. 10(b) the switch K is moved from position 'a' to 'b' at $t = 0$ having been in position 'a' for a long time before $t = 0$. Find the particular solution for (i) $i(t)$, $t \geq 0$ (ii) $U_2(t)$, $t \geq 0$. 7

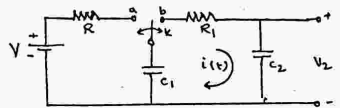


Fig. 10(b)

11. (a) Derive the condition for reciprocity in terms of ABCD parameters for the two port network. 7
 (b) Obtain z-parameters of a two port network shown in Fig. 11(b). 7

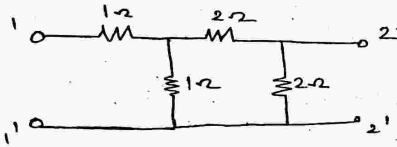


Fig. 11(b)

OR

12. (a) Find the voltage transfer ratio $G_{12}(s)$ for the network shown in Fig. 12(a). 7

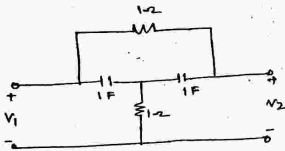


Fig. 12(a)

- (b) For the ladder network shown in Fig. 12(b), find $Z_{11}(s)$ and $G_{12}(s)$. 7

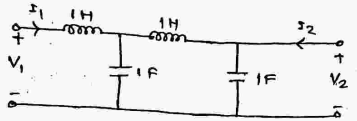


Fig. 12(b)