

Faculty of Engineering & Technology
First Semester B.E. (C.B.S.) Examination
BASIC ELECTRICAL ENGINEERING

Time : Two Hours]

[Maximum Marks : 40

INSTRUCTIONS TO CANDIDATES

- (1) All questions carry marks as indicated.
 - (2) Assume suitable data wherever necessary.
 - (3) Illustrate your answers wherever necessary with the help of neat sketches.
 - (3) Use of non-programmable calculator is permitted.
1. (a) Using Source Transformation, convert the circuit given below to a single voltage source in series with a resistor. Refer Fig. 1(a). 4

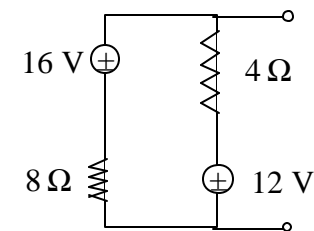


Fig. 1(a)

- (b) Using Superposition principle, find current (I) through 3Ω resistor. Refer Fig. 1(b). 6

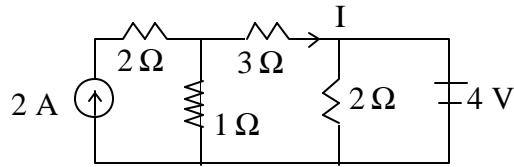


Fig. 1(b)

OR

2. (a) Find the value of Resistance 'R' shown in Fig. 2(a) when power consumed by the 12Ω resistor in the given circuit is 36 watts. 4

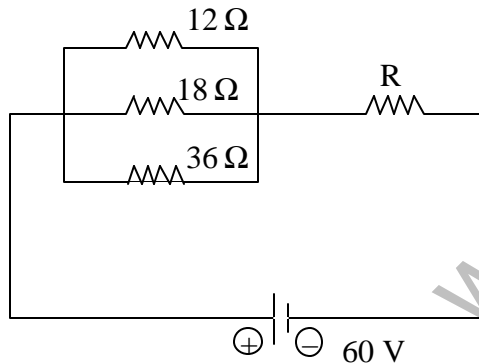


Fig. 2(a)

- (b) For the circuit in Fig. 2(b), using STAR-DELTA transformation, find source current (I_s). 6

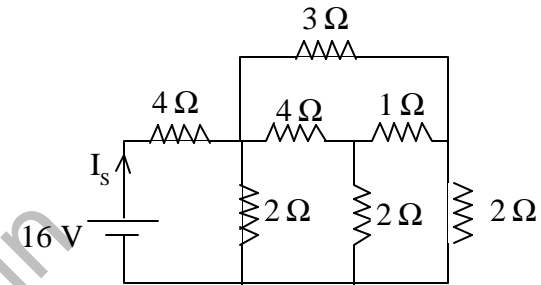


Fig. 2(b)

3. (a) Define and explain with neat sketch :

(i) Fringing

(ii) Useful flux

(iii) Leakage flux. 3

- (b) An iron ring of mean length of 600 mm and having a cross-sectional area of 4 cm^2 is required to produce a flux of 0.44 m.wb. Find the mmf to be provided by the coil wound on the ring.

If a saw cut of 1 mm wide is made in the

ring, how much extra mmf is required to maintain the same flux ? The points on $B-\mu_r$ curve are :

$B(\text{wb/m}^2)$	μ_r
0.8	2300
0.9	2150
1.0	2000
1.1	1815
1.2	1630
1.3	1365
1.4	1100

7

OR

4. (a) Draw complete hysteresis loop and explain :

- (i) Remanent flux density
- (ii) Residual flux
- (iii) Retentivity and
- (iv) Coercive force.

5

(b) A circular iron ring of mean circumference of 25 cm and cross-sectional area of 5 cm^2 has a radial saw cut of 1 mm in it. The ring is uniformly wound with a coil of 500 turns and current of 2 A in the coil produces a flux of $0.5 \times 10^{-3} \text{ wb}$ in the ring. Calculate the relative permeability of iron at this flux density. 5

5. (a) Determine the RMS value of sine wave rectifier output. 3

(b) A voltage of $200 \angle 25^\circ$ volt is applied to a circuit composed of 2 parallel branches, if the branch currents are $10 \angle 45^\circ \text{ A}$ and $20 \angle -30^\circ \text{ A}$, determine the KVA, KVAR and kW in each branch. Also calculate the P.F. of the combined load. 7

OR

6. (a) Derive the relationship between 'Power in Delta (P_D) and Power in Star (P_S)'. 4

(b) A balanced star connected load is supplied from a symmetrical 3ϕ , 410 V system. The current in each phase is 30 Amps and lags 30° behind the phase voltage. Find :

(i) R_p

(ii) X_p

(iii) Z_p

(iv) kW

(v) KVAR and

(vi) KVA. 6

(ii) Equivalent reactance referred to primary and secondary.

(iii) Total copper losses. 6

(b) Explain 'SHORT CIRCUIT TEST' on a single phase transformer with the help of neat sketch. 4

7. (a) What are the losses in the transformer ? Explain why the rating of transformer is in KVA. 4

(b) A 100 KVA, 1 KV/10KV, 50 Hz, 1-phase transformer has iron losses of 1100 watts and the copper loss with 5 A in high voltage winding is 400 watts. Calculate the efficiency at 25% of full load at (i) UPF and (ii) 0.8 pF lag, the output being maintained at 10,000 V. 6

OR

8. (a) A 15 KVA, 2200/110 V transformer has $R_1 = 1.75 \Omega$, $R_2 = 0.0045 \Omega$. The leakage reactances are $X_1 = 2.6 \Omega$ and $X_2 = 0.0075 \Omega$. Calculate :

(i) Equivalent resistance referred to primary and secondary.