

Faculty of Engineering & Technology
Fifth Semester B.E. (Electronics Engg.) (C.B.S.)
Examination
SWITCHING THEORY AND AUTOMATA

Time : Three Hours]

[Maximum Marks : 80

INSTRUCTIONS TO CANDIDATES

- (1) All questions carry marks as indicated.
- (2) Due credit will be given to neatness and adequate dimensions.
- (3) Assume suitable data wherever necessary.
- (4) Illustrate your answers wherever necessary with the help of neat sketches.

1. (a) Simplify the function using Kmap :

$$f(v, w, x, y, z) = \Sigma m(1, 2, 6, 7, 9, 13, 14, 15, 17, 22, 23, 25, 29, 30, 31)$$

7

- (b) Given the following three partitions on the set {a, b, c, d, e, f, g, h, i, j, k}

$$\pi_1 = \{\overline{a, b, c}; \overline{d, e}; \overline{f}; \overline{g, h, i}; \overline{j, k}\}$$

$$\pi_2 = \{ \overline{a, b}; \overline{c, g, h}; \overline{d, e, f}; \overline{i, j, k} \}$$

$$\pi_3 = \{ \overline{a, b, c, f}; \overline{d, e}; \overline{g, h, i, j, k} \}$$

(i) Find $\pi_1 + \pi_2$ and $\pi_1 \cdot \pi_2$

(ii) Find $\pi_1 + \pi_3$ and $\pi_1 \cdot \pi_3$ 6

OR

2. (a) Minimize the function using tabulation method :

$$f(w, x, y, z) = \Sigma m(0, 1, 2, 5, 7, 8, 9, 10, 13, 15).$$

7

(b) In an examination there are three problems A, B and C. In the following tabulation are the percentage of the students who received credit for solving one or more problems :

$$A : 40 \qquad A, B : 12 \qquad A, B, C : 4$$

$$B : 30 \qquad A, C : 8$$

$$C : 30 \qquad B, C : 6$$

What percent of the students received no credit at all for solving any of the three problems ? Use a Venn diagram. 6

3. (a) Decompose the function :

$$f(w, x, y, z) = \Sigma m(1, 3, 6, 10, 13, 15) \text{ about variables } y \text{ and } z \text{ by matrix method.}$$

7

(b) Determine whether the function is symmetric or not :

$$f(w, x, y, z) = \Sigma m(0, 3, 5, 10, 12, 15).$$

7

OR

4. (a) Decompose the function by employing the Expansion theorem and expanding function about the variables x and y :

$$f(w, x, y, z) = \Sigma m(0, 2, 3, 7, 9, 10, 11, 14).$$

7

(b) Design a minimal three output contact network to realize the functions shown below. Ten transfer contacts should be sufficient :

$$T_1(w, x, y, z) = \Sigma m(0, 1, 2, 4, 8)$$

$$T_2(w, x, y, z) = \Sigma m(3, 5, 6, 9, 10, 12)$$

$$T_3(w, x, y, z) = \Sigma m(7, 11, 13, 14, 15)$$

7

5. (a) Determine whether the function

$$f(x_1, x_2, x_3, x_4) = \Sigma m(0, 1, 3, 4, 5, 6, 7, 12, 13)$$

is a threshold function and if it is, find a weight threshold vector. 7

(b) Explain capabilities and limitations of threshold logic. 4

(c) What is unate function ? 2

OR

6. (a) Given the switching function :

$$f(x_1, x_2, x_3, x_4) = \Sigma m(2, 3, 6, 7, 10, 12, 14, 15).$$

find a minimal threshold logic realization. 10

(b) Explain Elementary property of threshold element.

3

7. Design Moore circuit for sequence 1001 in which overlapping is allowed. Implement the function using JK flip flop. 14

OR

8. Design an asynchronous sequential circuit with two inputs x_1 and x_2 and one output z . The initial input state is $x_1 = x_2 = 0$. The circuit output is to be 1 if and only if the input state is $x_1 = x_2 = 1$ and the preceding input state is $x_1 = 0, x_2 = 1$. 14

9. (a) For the machine given in the table below, find the equivalent partitions and a corresponding reduced machine in standard form :

PS	NS		Z
	x = 0	x = 1	
A	H	B	0
B	F	A	0
C	G	D	0
D	E	C	1
E	A	C	0
F	C	D	0
G	B	A	0
H	D	B	0

7

- (b) Draw the homing tree and find the shortest homing sequence and the response of machine to homing sequence :

PS	NS, Z	
	x = 0	x = 1
A	B, 0	D, 0
B	A, 0	B, 0
C	D, 1	A, 0
D	D, 1	C, 0

6

OR

10. (a) For the machine given below design an autonomous clock :

PS	NS		Z	
	x = 0	x = 1	x = 0	x = 1
A	D	C	0	1
B	C	D	0	0
C	E	F	0	1
D	F	F	0	0
E	B	A	0	1
F	A	B	0	0


7

- (b) Construct an Adaptive distinguishing experiment for the machine given below :

PS	NS, Z	
	x = 0	x = 1
A	C, 0	A, 1
B	D, 0	C, 1
C	B, 1	D, 1
D	C, 1	A, 0

6

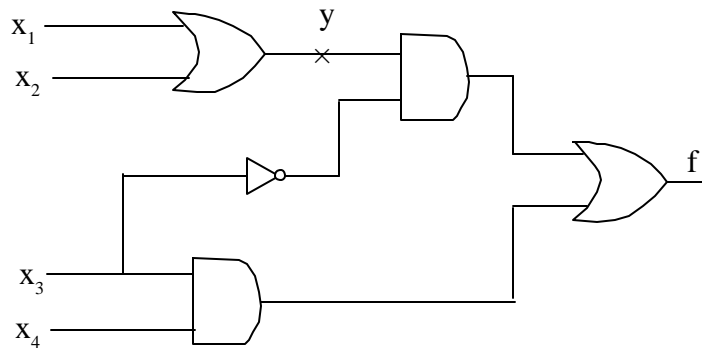11. (a) For the following combinational circuit, detect s-a-0 and s-a-1 at x_3 by Boolean difference :



7

- (b) Explain in brief advantages and limitations of path sensitizing method for fault detection. 6

OR

12. (a) Find 'a' test and 'b' test for the combinational logic circuit which realizes the function :

$$f(w, x, y, z) = \bar{w}\bar{y} + \bar{y}z + wxz + xy\bar{z}. \quad 7$$

- (b) What are Hazards ? Explain different types of Hazards that occur in digital circuit. 6