

9. (A) What are the various configurations of differential amplifier ? Also draw its diagram. 7
 (B) What is the need of level shifting stage ? Also write the various level shifting techniques available. 6

OR

10. (A) Explain :
 (a) Constant current bias
 (b) Current mirror circuit. 8
 (B) What is the use of swamping resistors in DIBO differential amplifier ? 5
11. (A) Convert the following :
 (i) $(257.556)_8 = (?)_2$
 (ii) $(7896.1225)_{10} = (?)_{16}$
 (iii) $(111001.1010)_2 = (?)_{10}$
 (iv) $(26AF.78C) = (?)_2$. 8
 (B) Realize the expression :
 $Y = ABC + AB + AC + B + AB$ using basic gates after minimizing it. 6

OR

12. (A) What are the universal gates ? Why they are called so ? 4
 (B) State and prove DeMorgan's laws. 6
 (C) Develop 4 bit gray code. 4

Faculty of Engineering & Technology
 Third Semester B.E. (Electrical Engg.)
 (C.B.S.) Examination

ELECTRONIC DEVICES & CIRCUITS

Time : Three Hours] [Maximum Marks : 80

INSTRUCTIONS TO CANDIDATES

- (1) All questions carry marks as indicated.
 (2) Answer **SIX** questions.
 (3) Assume suitable data wherever necessary.
 (4) Illustrate your answers wherever necessary with the help of neat sketches.
1. (A) Draw VI characteristics of PN-junction diode and explain how it depends upon temperature. 6
 (B) Draw circuit diagram of full wave rectifier and hence obtain the expression for :
 (i) Peak current
 (ii) Ripple factor
 (iii) Efficiency. 8


OR

2. (A) An AC voltage of 230 V is applied to half wave rectifier circuit through a transformer of turns ratio 10 : 1. The load resistance is 1 K and diode internal resistance is 20 Ω . Determine dc output power, efficiency and PIV. 7

- (B) Explain the difference between Zener and Avalanche breakdown in diodes. 4
- (C) Explain voltage doubler. 3
3. (A) What is the need of biasing ? Draw and explain voltage divider bias method of transistor biasing. 7
- (B) Draw input and output characteristics of CE configuration and explain why CE configuration of transistor is mostly used. 6

OR

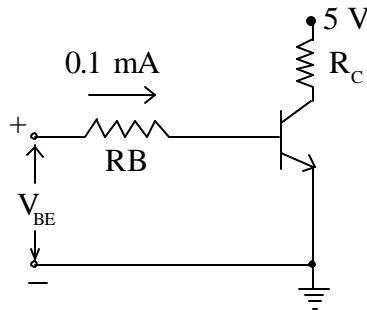4. (A) Explain with necessary circuit diagram how transistor can be used as a switch. 6
- (B) In the circuit shown below, what should be the minimum value of β such that transistor is in saturation ? Assume $V_{CE(sat)} = 0.2 \text{ V}$, $R_C = 1 \text{ K}\Omega$, $R_B = 10 \text{ K}\Omega$. 7



5. (A) Differentiate between class A, B, AB and C power amplifier. 6

- (B) What do you mean by positive and negative feedback ? What are the advantages of negative feedback ? 7

OR

6. (A) Draw and explain the working of class B push-pull power amplifier and determine its efficiency. 5
- (B) For class A power amplifier the operating point is located at $I_C = 250 \text{ mA}$ and $V_{CE} = 8 \text{ V}$. Due to input signal the output collector current goes between 450 mA and 40 mA. The V_{CE} swings between 15 V and 1 V. Determine :
- The output power delivered
 - The input power
 - Collector efficiency
 - Power dissipated by transistor. 8
7. (A) What is Barkhausen criteria for sustaining oscillations ? Explain. 6
- (B) Explain the working of RC phase shift oscillator with neat diagram and derive the expression for its frequency of oscillation. 7

OR

8. (A) With the help of neat diagram, explain the working of JFET. Also draw and explain static drain characteristics. 7
- (B) A JFET has $V_p = -4.5 \text{ V}$, $I_{DSS} = 10 \text{ mA}$, $I_D = 2.5 \text{ mA}$, Determine the transconductance. 6

NTK/KW/15/7314

NTK/KW/15/7314

**Faculty of Engineering & Technology
Third Semester B.E. (Electrical Engg.)
(C.B.S.) Examination**

ELECTRONIC DEVICES & CIRCUITS

Note :— MSS says Paper-SIVIM, but not mentioned in Envelope. Press has followed Envelope. Please check.

**Faculty of Engineering & Technology
Third Semester B.E. (Electrical Engg.)
(C.B.S.) Examination**

ELECTRONIC DEVICES & CIRCUITS

Note :— MSS says Paper-SIVIM, but not mentioned in Envelope. Press has followed Envelope. Please check.

NTK/KW/15/7314

NTK/KW/15/7314

**Faculty of Engineering & Technology
Third Semester B.E. (Electrical Engg.)
(C.B.S.) Examination**

ELECTRONIC DEVICES & CIRCUITS

Note :— MSS says Paper-SIVIM, but not mentioned in Envelope. Press has followed Envelope. Please check.

**Faculty of Engineering & Technology
Third Semester B.E. (Electrical Engg.)
(C.B.S.) Examination**

ELECTRONIC DEVICES & CIRCUITS

Note :— MSS says Paper-SIVIM, but not mentioned in Envelope. Press has followed Envelope. Please check.