

- (b) Find transfer function $\frac{I_2}{V_1}$ for the Network shown in Fig. 10(b). 7

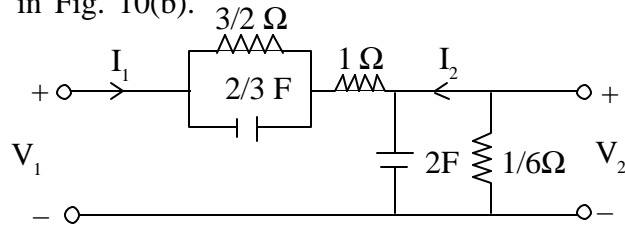


Fig. 10(b)

11. (a) Define ABCD parameters and derive the condition for reciprocity in terms of ABCD parameters. 7
 (b) Find the Z-parameter of the Network shown in Fig. 11(b). 7

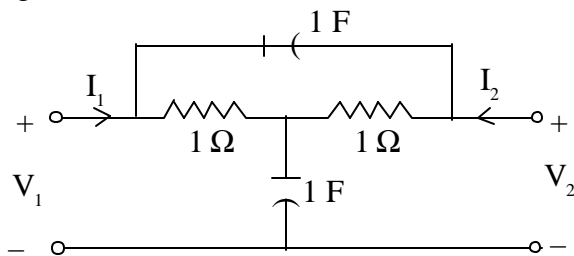


Fig. 11(b)

OR

12. (a) Compare series and parallel resonant circuit. 6
 (b) A 400 V, 3 phase supply feeds an unbalanced three wire star-connected load. The branch impedances of the load are $Z_R = (4 + j8)\Omega$. $Z_Y = (3 + j4)\Omega$ and $Z_B = (15 + j20)\Omega$. Find the line current and voltage across each phase impedance. Assume RBY as phase sequence. 8

Faculty of Engineering & Technology
Third Semester B.E. (Electrical Engg.)
(C.B.S.) Examination
NETWORK ANALYSIS

Time : Three Hours] [Maximum Marks : 80

INSTRUCTIONS TO CANDIDATES

- (1) All questions carry marks as indicated.
 - (2) Due credit will be given to neatness and adequate dimensions.
 - (3) Assume suitable data wherever necessary.
 - (4) Illustrate your answers wherever necessary with the help of neat sketches.
 - (5) Use of non-programmable calculator is permitted.
1. (a) Using source transformation, convert the ckt. shown in Fig. 1(a) into single voltage source and single resistance. 6

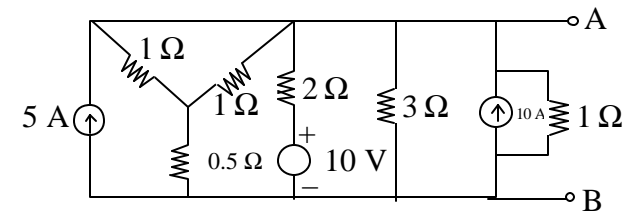


Fig. 1(a)

- (b) Determine the Mesh current I_1 , I_2 and I_3 in the Network of Fig. 1(b). 7

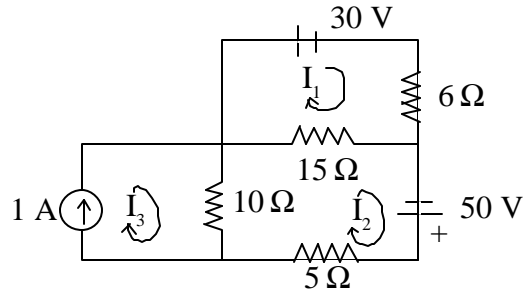


Fig. 1(b)

OR

2. (a) Determine the magnitude of voltage source $V_1(t)$ which results of 20 volt across 5Ω resistance as shown in Fig. 2(a). 7

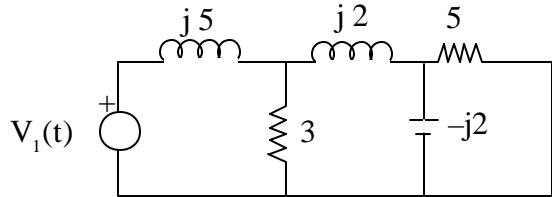


Fig. 2(a)

- (b) For the Network shown in Fig. 2(b), write Mesh equations in matrix form. 6

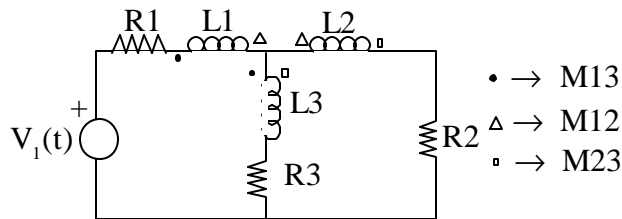


Fig. 2(b)

3. (a) Find the voltage V , which makes the current in 10Ω resistance is zero using nodal analysis. 6

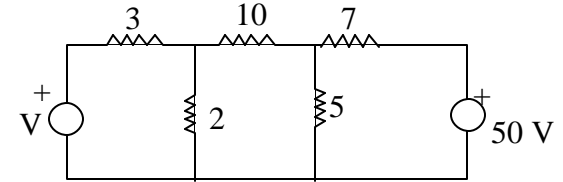


Fig. 3(a)

- (b) Write the matrix form of the nodal equation for the Network shown. 7

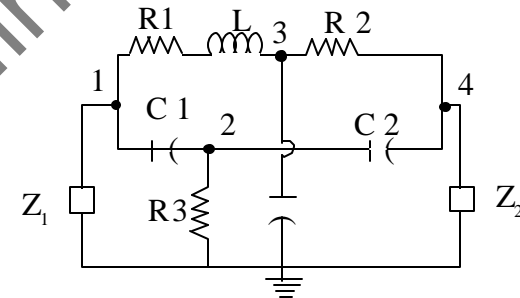


Fig. 3(b)

OR

4. (a) Define Dual Network. Draw the dual of the following Network. Write the condition satisfied by Dual Network. 6

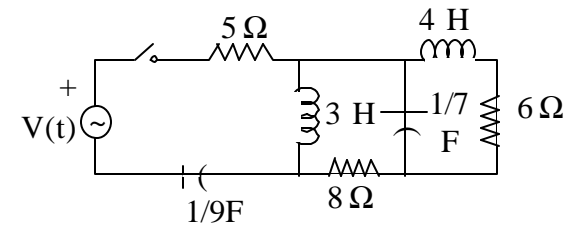


Fig. 4(a)

- (b) Using nodal analysis for the 'Fig. 4(b)', find the power factor of source V_A and V_B . 7

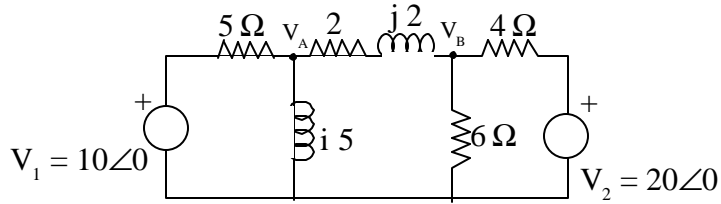


Fig. 4(b)

5. (a) In the Network of Fig 5(a) shown below; determine V_b by principle of Superposition. 7

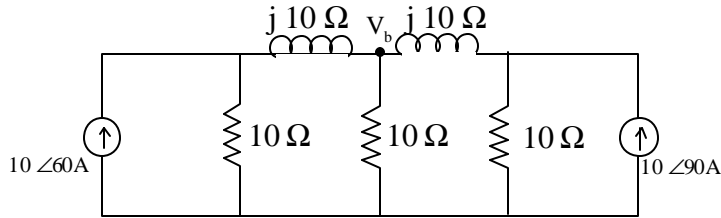


Fig. 5(a)

- (b) Find out the current flowing through branch AB of Network shown in Fig. 5(b) by applying Norton's theorem and hence find Thevenin's equivalent network. 7

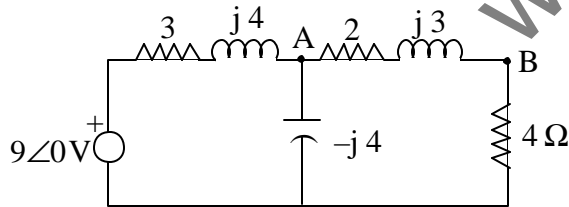


Fig. 5(b)

OR

6. (a) Find the current I and verify the reciprocity theorem for the Network shown in Fig. 6(a). 7

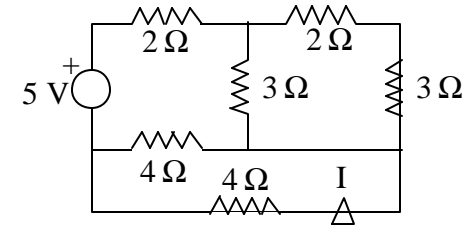


Fig. 6(a)

- (b) For the Network shown in Fig. 6(b) the 5 Ω resistor is changed to 8 Ω. Determine the resulting change in current ΔI through $(3+j4)\Omega$ impedance branch using Compensation theorem. 7

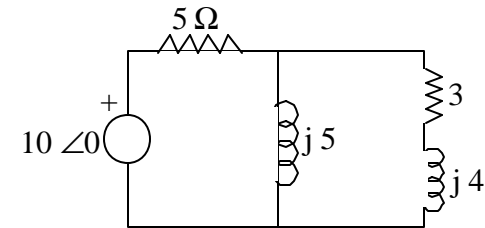


Fig. 6(b)

7. (a) In the Network of Fig. 7(a), the switch is opened at $t = 0$, find $i_1(t)$. 7

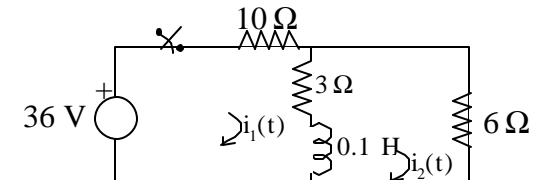


Fig. 7(a)

- (b) Derive the expression for the impulse response of series RC Network using Laplace transform.

6

OR

8. (a) In the Network of Fig. 8(a) was initially in the steady state with the switch in the position a. At $t = 0$ the switch goes from a to b. find expression for voltage $V(t)$ for $t > 0$.

7

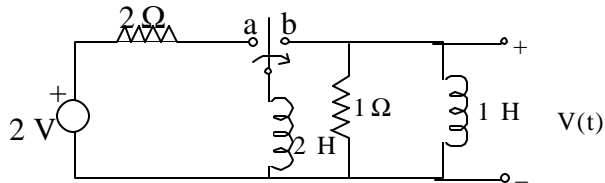


Fig. 8(a)

- (b) Find the Laplace transform of the waveform shown in Fig 8(b).

6

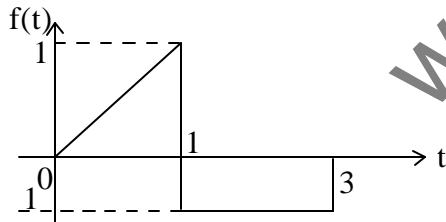


Fig. 8(b)

9. (a) Find the driving point admittance function of the Network shown.

4

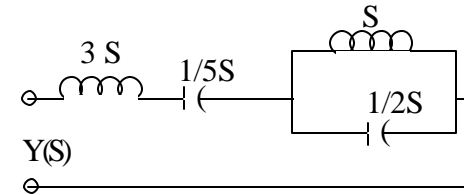


Fig. 9(a)

- (b) Define the following terms :

- (1) Driving point function
 - (2) Transfer function
 - (3) Current gain.
- (c) The voltage $V(s)$ of a Network is given by $V(s) = \frac{3s}{(s+2)(s^2+2s+2)}$. Plot its pole-zero diagram and hence obtain $V(t)$ from pole-zero diagram.

3

6

OR

10. (a) Determine the voltage transfer function $\frac{V_2}{V_1}$ for the Network shown in Fig. 10(a).

6

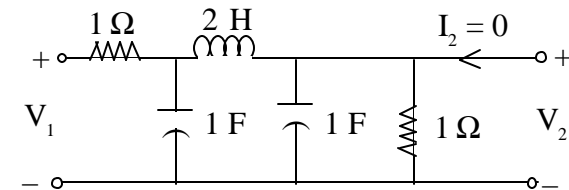


Fig. 10(a)