

Faculty of Engineering & Technology
First Semester B.E. (C.B.S.) Examination
BASIC ELECTRICAL ENGINEERING
Paper—IV

Time—Two Hours]

[Maximum Marks—40

INSTRUCTIONS TO CANDIDATES

- (1) All questions carry marks as indicated.
 - (2) Assume suitable data wherever necessary.
 - (3) Illustrate your answers wherever necessary with the help of neat sketches.
 - (4) Use of non-programmable calculator is permitted.
1. (a) What do you understand by 'an ideal voltage source' and an 'ideal current source'? Draw the circuit symbol and characteristics. 4
- (b) Determine the circuit current drawn from 5 V battery by 'STAR-DELTA' transformation as shown in 'Fig. 1(b)'. 6

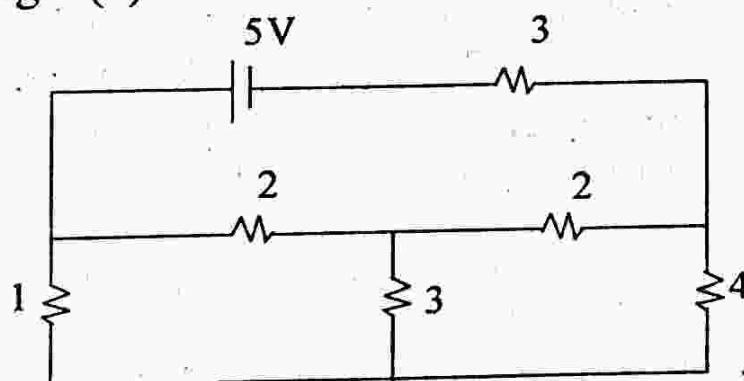


Fig. 1(b)

OR

2. (a) Determine the current ' I_x ' through $10\ \Omega$ resistor as shown in 'Fig. 2(a)' using SUPERPOSITION THEOREM.

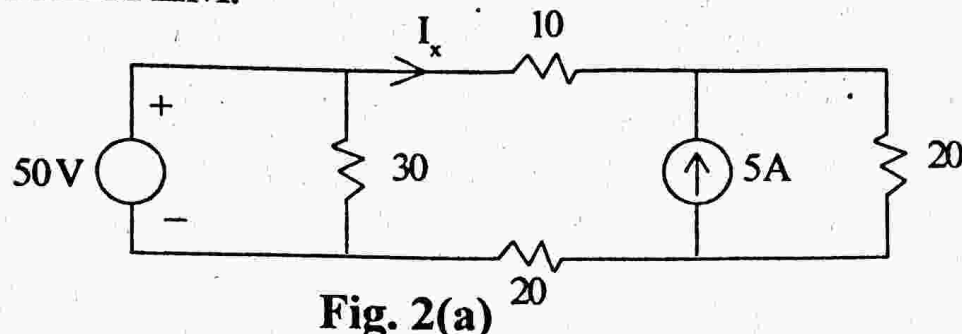


Fig. 2(a)

6

- (b) A resistance of ' $R\ \Omega$ ' is connected in series with a parallel combination of $8\ \Omega$, $12\ \Omega$ and $24\ \Omega$. The total power dissipated on the circuit is $80\ \text{W}$, when the applied voltage is $20\ \text{V}$. Calculate R .

4

3. (a) Define the terms :

- (i) Permeability
- (ii) Relative permeability
- (iii) Reluctance
- (iv) Permeance.

4

- (b) An iron ring with a mean length of magnetic path of $20\ \text{cm}$ and of small cross-sectional area has an air gap of $1\ \text{mm}$ long. A current of $1\ \text{A}$ in a coil of 440 turns wound uniformly over the ring produces a flux density of $16\pi \times 10^{-3}\ \text{T}$. Neglecting leakage and fringing, determine relative permeability of iron. Assume $\pi = 3.14$.

6

OR

4. (a) Explain in what respect a magnetic circuit differs from an electric circuit.

3

- (b) A cast steel of mean diameter 30 cm having a cross-sectional area of 5 cm^2 is uniformly wound with 500 turns. Determine the magnetising current required to establish a flux of $5 \times 10^{-4} \text{ Wb}$:

- (i) with no air gap
(ii) with a radial air gap of 1 mm.

The magnetisation curve of cast steel is given below :

B(Wb/m ²)	0.4	0.6	0.8	1	1.2
H(AT/m)	300	400	600	900	1250

7

5. (a) In a series RLC circuit the current is seen to be lagging the voltage. What does it mean ? Draw the phasor diagram. Also write the equations of voltage and current in alternating form. 4
- (b) A coil has a resistance of 10Ω and draws a current of 5A when connected across a 100 V , 60Hz supply source. Determine :
- (i) inductance of the coil
(ii) power factor of the circuit and nature
(iii) equation of current in alternating form
(iv) the active and reactive power. 6

OR

6. (a) Derive the relationship between line current and phase current for 3 phase Delta connected system with phasor diagram. 5

- (b) A balanced 3-phase, STAR-connected, 210 kW load takes a leading current of 160 A when connected across a balanced 3-phase, 1.1 kV, 50 Hz supply. Find the load circuit parameters per phase. 5
7. (a) The primary and secondary windings of 500-kVA, 11-kV/415-V, single-phase transformer have resistances of 0.42Ω and 0.019Ω , respectively. Its core losses are 2.9 kW. Calculate :
- (i) copper loss at full load
 - (ii) efficiency of transformer at full load, 0.8 p.f. lag
 - (iii) efficiency of transformer at 70% of full load, upf.
 - (iv) the load at which the maximum efficiency occurs. 8
- (b) Explain various features of an 'Ideal' transformer. 2

OR

8. (a) Justify :
- In transformer, O.C. test gives Iron losses and S.C. test gives Cu-losses. 2
- (b) Derive the condition for maximum efficiency of transformer. 4
- (c) A transformer on no load takes 1.5 A at a power factor of 0.2 lagging when its primary is connected to a 50-Hz, 230-V supply. The transformation ratio is $1/3$. Determine the primary current when the secondary is supplied a current of 40A at a p.f. of 0.8 lagging. Also find the power factor and its nature. 4