

**NTK/KW/15–7336**

**Third Semester B. E. (Computer Engg.)  
(CBS) Examination**

**DIGITAL ELECTRONICS**

Time : Three Hours ]

[ Max. Marks : 80

- N. B. : (1) All questions carry marks as indicated.  
(2) Answer **Six** questions.  
(3) Assume suitable data wherever necessary.  
(4) Illustrate your answers wherever necessary with the help of neat sketches.

1. (a) Show that :—  
(i)  $\overline{A}BC + B + B\overline{D} + AB\overline{D} + \overline{A}C = B + C$   
(ii)  $(A + \overline{B} + \overline{A}\overline{B})(AB + \overline{A}C + BC) = AB + \overline{A}\overline{B}C$  4  
(b) Convert the following function to standard SOP form.  $F(A, B, C, D) = AB + AC + C + AD$  4  
(c) Explain how transistor acts as a switch. 5

**OR**

2. (a) Perform the following conversions :—  
(i)  $(275.625)_{10} = (?)_2$   
(ii)  $(A72E)_{16} = (?)_8$   
(iii)  $(1100110.1001)_2 = (?)_{16}$   
(iv)  $(111000)_{\text{gray}} = (?)_{\text{binary}}$  8

NTK/KW/15–7336

Contd.

- (b) Define :—
- (i) Fan-in
  - (ii) Fan-out
  - (iii) Propagation delay. 5

3. (a) Design an Excess -3 to BCD code converter using minimum number of NAND gates only. 7
- (b) Design 5:32 decoder by using 3:8 decoder and 2:4 decoder. 7

**OR**

4. (a) Design BCD to seven segment display code converter. 7
- (b) Implement the following function using 8:1 MUX  
:  $F(A, B, C, D) = \sum m(2, 4, 6, 7, 9, 10, 11, 12, 15)$  7
5. Minimize the following function using k-map and realize using logic gates.
- (i)  $f(A, B, C, D, E) = \sum m(1, 4, 6, 10, 20, 22, 24, 26) + \sum d(0, 11, 16, 17)$  7
  - (ii)  $F(A, B, C, D) = \pi m(0, 3, 4, 5, 6, 7, 11, 13, 14, 15)$  6

**OR**

6. (a) Design NOR gate circuit for the function F where.  
 $F(A, B, C, D, E) = \pi M(1, 2, 4, 9, 10, 13, 17, 23, 27)$   
 $d(6, 12, 15, 20, 25, 30)$  7

(b)  $F(A, B, C, D) = \Sigma M(2, 3, 5, 7, 9, 11, 12, 13, 14, 15)$   
design using NAND gates. 6

7. (a) What is race-around condition in JK flip-flop ?  
Also explain how it is overcome. 7

(b) Convert the following :—

(i) Jk flip-flop to D flip-flop.

(ii) SR flip-flop to T flip-flop. 7

**OR**

8. (a) Explain in brief ROM, PROM, EPROM and E<sup>2</sup>PROM. 8

(b) Discuss in brief semiconductor memory organization and its operation. 6

9. (a) Design a MOD-5 synchronous counter using T flip-flop. 7

(b) Explain the working of twisted ring counter with suitable example. 6

**OR**

10. (a) Write a note on Johnson counter. 5

(b) What do you understand by parallel and serial shifting in case of shift register ? Explain with proper diagram. 8

11. (a) Explain full adder circuit using two half adder circuit. 7

(b) Write short note on ALU. 6

**OR**

12. (a) Design astable multivibrator using logic gates.  
Explain its operations. 7

(b) Design 4 bit adder using single bit full adders. 6