

Faculty of Engineering & Technology  
 Third Semester B.E. (Electronics Engg./ET/EC)  
 (C.B.S.) Examination  
**NETWORK ANALYSIS AND SYNTHESIS**

Time—Three Hours]

[Maximum Marks—80

**INSTRUCTIONS TO CANDIDATES**

- (1) All questions carry marks as indicated.
  - (2) Assume suitable data wherever necessary.
  - (3) Illustrate your answers wherever necessary with the help of neat sketches.
  - (4) Use of Non-Programmable calculator is permitted.
1. (a) Find the current  $J_1$  and  $J_2$  due to d.c. source in the network shown below in 'Fig. 1(a)'.

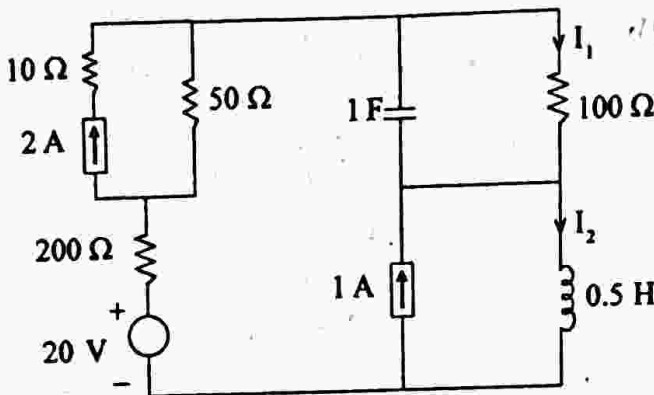


Fig. 1(a)

6

- (b) Write the set of independent mesh equations for the network shown below in Fig. 1(b):

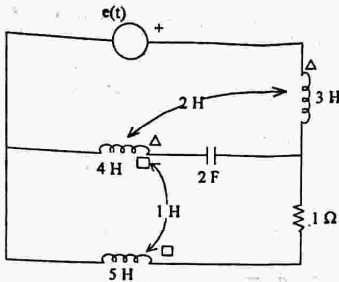


Fig. 1 (b)

7

OR

2. (a) In the network shown in 'Fig. 2(a)', determine the voltage  $\bar{V}_b$  which results in zero current through  $(2 + j3) \Omega$  impedance. Use Nodal analysis.

32.26 L 29.80

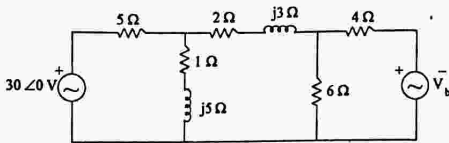


Fig. 2 (a)

7

MIS-49262

2

Contd.

- (b) Define duality. What are the conditions for duality? Obtain the dual of the network shown in 'Fig. 2(b)'.

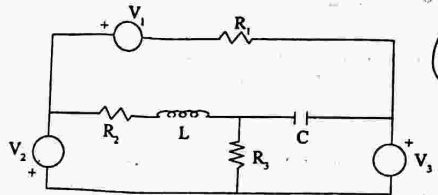


Fig. 2 (b)

6

3. (a) What should be the value of ' $Z_L$ ', connected across A and B in 'fig. 3(a)' so that it will draw the maximum power. Also calculate the maximum power.

1

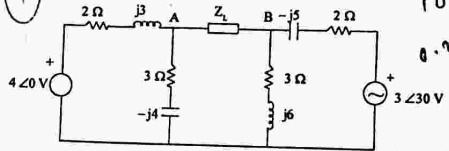


Fig. 3 (a)

10.29 L-1.03  
0.21 L 60.14

7

- (b) In the network shown in 'Fig. 3(b)', if resistance ' $R_1$ ' is decreased by 10%, find the change in current

MIS-49262

3

Contd.

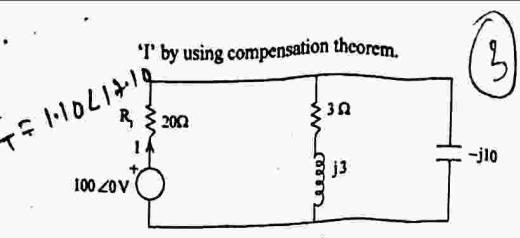


Fig. 3 (b) 7

OR

4. (a) In the network shown in 'Fig. 4(a)' find 'I' and verify reciprocity theorem.

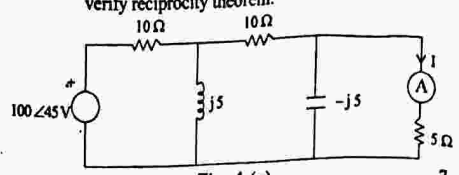


Fig. 4 (a) 7

(b) Obtain Thevenin's and Norton's equivalent across the terminals A and B of the network shown in 'Fig. 4(b)'.

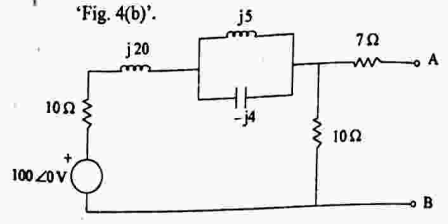


Fig. 4 (b) 7

(4) (a) For R-L-C series circuit derive the expression for resonant frequency and show the variation of  $R$ ,  $X_L$ ,  $X_C$ ,  $(X_L - X_C)$ ,  $Z$  and  $I$  on the same graph. 7

(6) Series RLC circuit is resonant at 1 Mega Cycles/sec. Its bandwidth is 5000 cycles/sec. and impedance at resonance is 50 Ω. Determine the values of R, L and C. OR  $1.59 \times 10^{-3} 6$   
 $1.59 \times 10^{-1} 7$

6. (a) Compare series and parallel resonance in A.C. circuit. 6

(b) Explain the meaning of half power frequencies for series RLC circuit. Also calculate the half power frequencies, resonant frequency, bandwidth and Q-factor for RLC series circuit with  $R = 0.2 \Omega$ ,  $L = 100 \text{ mH}$ , and  $C = 50 \mu\text{F}$ . 7

(7) (a) Design constant K low pass 'T' and 'π' sections of filter having cut-off frequency 3000 Hz and nominal characteristic impedance of 600 Ω. Also find the frequency at which filter offers attenuation of 16 db. 7

(b) Explain the meaning of band pass and band stop filter. Also design a prototype band pass filter having cut-off frequency of 2000 Hz and 5000 Hz. The nominal characteristic impedance is 600 Ω. 7

$0.065$   
 $0.01$

8. (a) Draw the equivalent circuit of transmission line and write the equations for voltage and current. 7  
 (b) Explain the design procedure for high pass filters. 7
9. (a) Find the continuous solution for  $i_1(t)$  and  $i_2(t)$  of Fig. 9(a), if the switch 'K' is closed at  $t = 0$ . Assume the networks to be initially relaxed.

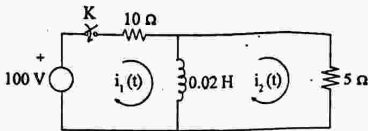


Fig. 9 (a) 7

- (b) Synthesize the waveform of 'Fig. 9(b)' and obtain its Laplace Transform :

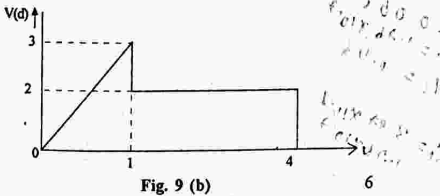


Fig. 9 (b) 6

MIS-49262

6 d d

Contd.

- OR
10. (a) Find the Laplace transform of periodic waveform shown in Fig. 10(a).

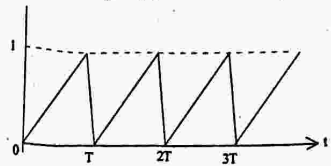


Fig. 10 (a) 6

- (b) Find the particular solution for the current  $i(t)$ , of Fig. 10 (b), when the switch is moved from 'x' to 'y' at time  $t = 0$ ; steady state is being previously established in the circuit.

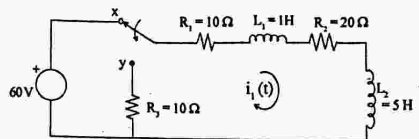


Fig. 10 (b) 7

11. (a) Express Z-parameters in terms of :  
 (i) ABCD parameters  
 (ii) h-parameters.

MIS-49262

7

Contd.

- (b) For the network shown 'Fig. 11(b)', find  $Y_{12}(S)$  and plot its poles and zeros.

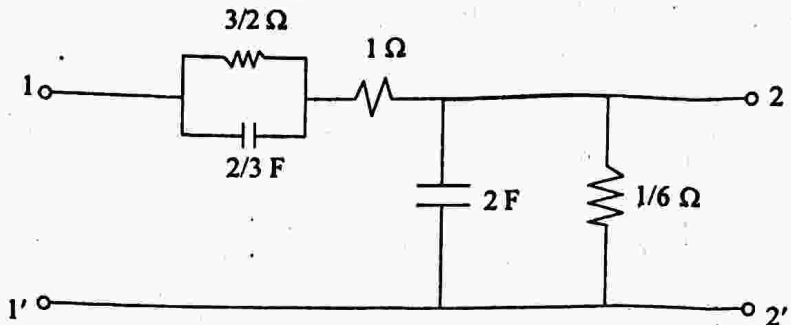


Fig. 11(b)

7

OR

12. (a) Define ABCD parameters and obtain the condition for reciprocity in terms of ABCD parameters. 7
- (b) Find the voltage transfer function  $G_{12}(S)$  for the network shown in Fig. '12(b)'.

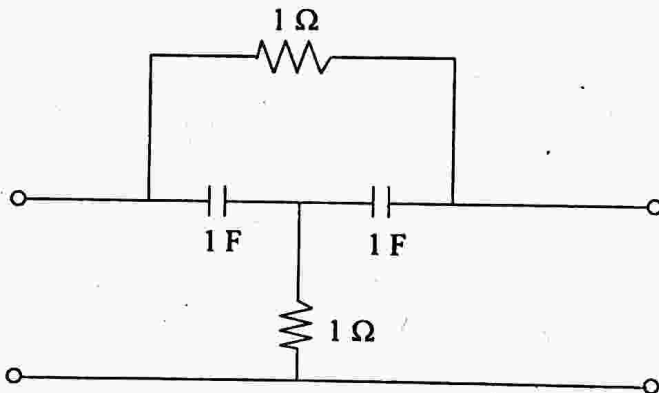


Fig. 12(b)

6