

Faculty of Engineering & Technology

Third Semester B.E. (Electronics Engg./ET/EC)

(C.B.S.) Examination

ELECTRONIC DEVICES AND CIRCUITS

Time—Three Hours]

[Maximum Marks—80

INSTRUCTIONS TO CANDIDATES

- (1) All questions carry marks as indicated.
- (2) Answer **SIX** questions.
- (3) Due credit will be given to neatness and adequate dimensions.
- (4) Assume suitable data wherever necessary.
- (5) Illustrate your answers wherever necessary with the help of neat sketches.
- (6) Use of non-programmable calculator is permitted.

SUMMER-15

1. (a) Compare transition capacitance and diffusion capacitance. 3
- (b) Explain effect of temperature on diode current. 3
- (c) Two similar P-N junction Ge diodes are connected in series opposing A 6V battery is impressed upon the series arrangement. Find the voltage across each junction at room temperature. The breakdown voltage is greater than 6V. 7


OR

2. (a) Explain bridge rectifier with the help of diode current, output current and output voltage waveform. Explain peak inverse voltage for this circuit and derive expression for average current. 6
- (b) Show that maximum rectification efficiency of full wave rectifier is 81.2%. 7
3. (a) Explain how BJT works as an amplifier. 5

(Contd.)

S-15

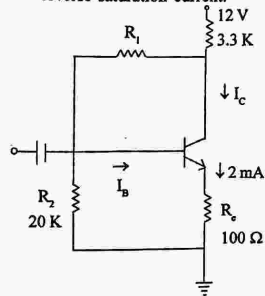- (b) If $\alpha = 0.98$ and $V_{BE} = 0.7V$, find R_1 in the circuit shown for an emitter current of 2 mA. Neglect the reverse saturation current. 6



- (c) Compare different regions of BJT with respect to their dimension and doping level. 3

OR

4. (a) What is the necessity of biasing for BJT circuit? 4
- (b) Define Stability factors. 3
- (c) Explain self bias circuit and derive its equation of stability. 7


MMW-9694

3

(Contd.)

5-15

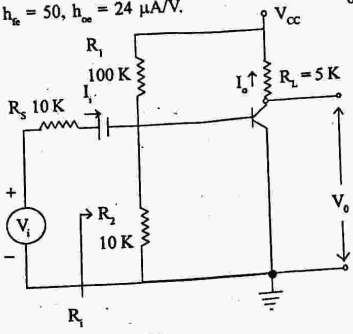5. (a) Compare CE, CB and CC configurations. 5
 (b) Calculate $A_i = \frac{I_o}{I_i}$, A_v , A_{v_s} , R_o and R_i for given circuit. Assume $h_{ie} = 1100 \Omega$, $h_{re} = 2.5 \times 10^{-4}$, $h_{fe} = 50$, $h_{oe} = 24 \mu A/V$. 8



OR

6. (a) Explain advantages of negative feedback amplifiers in detail. 6
 (b) When negative feedback is applied to an amplifier having gain 100, the overall gain falls to 50.
 (i) Calculate the fraction of output voltage feedback.

5-15

- (ii) If this feedback fraction is maintained, calculate the value of the amplifier gain required if the overall gain is to be 75. 7
7. (a) Explain crystal oscillator. Derive expression of resonant frequencies. 7
 (b) A Hartley oscillator is designed with $L_1 = 2 \text{ mH}$, $L_2 = 20 \mu\text{H}$ and a variable capacitance. If the frequency of oscillation is varied between 0.9 MHz and 2.1 MHz, find the range of capacitance values. 6
- OR
8. (a) Explain working of astable multivibrator with its circuit diagram. 6
 (b) Explain Barkhausen's criteria of oscillation. 3
 (c) Draw and explain working of RC phase shift oscillator. 4
9. (a) Explain Class B push pull power amplifier. Calculate its conversion efficiency. 6
 (b) Calculate the harmonic distortion for an output signal of a power amplifier having fundamental amplitude of 2.5 V, second harmonic amplitude of 0.25 V, third of 0.15 V and fourth of 0.05 V. 7

OR

S-15

10. (a) What is harmonic distortion in power amplifiers and how it can be reduced? 6
- (b) With a load of 4Ω , a push pull amplifier takes 3.25 A from the d.c. supply, with the sinusoidal signal. If $V_{CC} = 24$ volts, find the conversion efficiency. 7
11. (a) Explain static drain characteristics of JFET. 5
- (b) For JFET, if $I_{DSS} = 20$ mA, $V_{GS(off)} = -5$ V and $g_{m0} = 4$ ms, determine the transconductance for $V_{GS} = -4$ V and find I_D at this point. 6
- (c) How JFET works as voltage variable resistance? 3

OR


12. (a) Compare BJT and FET. 4
- (b) The amplifier stage shown uses n-channel FET with $I_{DSS} = 1$ mA and $V_p = -1$ V. Find the resistance R_1 if the quiescent drain to ground voltage is 10 V. 6

MMW-9694

6

(Contd.)

S-15

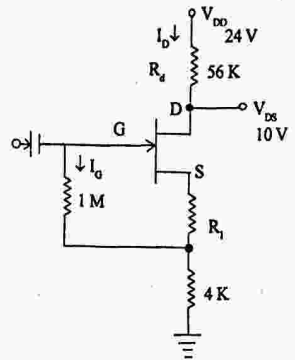

- (c) Explain the enhancement effect in MOSFET. 4

MMW-9694

7

6050