

**NTK/KW/15/7301/7306**

**Faculty of Engineering & Technology**  
**Third Semester B.E. (Electronics Engg.)/ET/EC**  
**(C.B.S.) Examination**

**ELECTRONIC DEVICES & CIRCUITS**

Time : Three Hours]

[Maximum Marks : 80

**INSTRUCTIONS TO CANDIDATES**

- (1) All questions carry marks as indicated.
- (2) Due credit will be given to neatness and adequate dimensions.
- (3) Assume suitable data wherever necessary.
- (4) Illustrate your answers wherever necessary with the help of neat sketches.
  - (a) Explain the transition and diffusion capacitance in p-n junction diode. 6
  - (b) Two p-n junction Ge diodes are connected as shown in Fig 1(b). Find the voltage across each diode if the breakdown voltage is greater than 5 V.

What will be the current in the circuit if breakdown voltage is 4.9 V ?  $I_o = 5 \mu\text{A}$ . 7

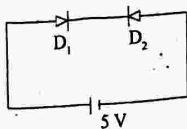


Fig. 1(b)

OR

2. (a) Explain the working of full wave bridge rectifier with the help of waveforms and circuit diagram. 7
- (b) Show that maximum rectification efficiency of half wave rectifier is 40.6%. 6
3. (a) Explain Early effect or Base width modulation. 6
- (b) Find if the transistor is in active or saturation region. Assume  $\beta = 100$  and neglect junction voltages.
  - (i) Calculate  $V_o$  for the circuit.

(ii) What is the minimum value of  $\beta$  that will saturate the transistor? 8

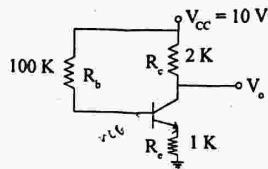


Fig. 3(b)(ii)

OR

4. (a) Explain thermal runaway in a power transistor. 3
- (b) What are the factors that affect stability of operating point? 5
- (c) Explain self bias circuit and derive expression for its stability factor. 6
5. (a) What is small signal condition? Why hybrid parameters are used in analyzing low frequency network? 4
- (b) Find  $A_v$ ,  $Z_i$ ,  $A_v$  and  $A_{v_s}$  for the circuit shown Fig. 5(b).

$$h_{ie} = 1.1 \text{ K}, \quad h_{re} = 2.5 \times 10^{-4}$$

$$h_{fe} = 50, \quad \frac{1}{h_{oc}} = 40 \text{ K}$$

9

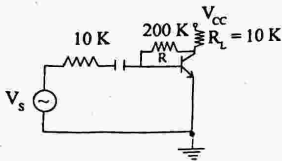


Fig. 5(b)

OR

6. (a) Explain the following feedback topologies and draw the practical circuits :
- Current series feedback
  - Voltage shunt feedback.
- (b) An amplifier without feedback gives 30 V with 10% second harmonic distortion when input is 0.025 V.
- If 1.5% of output is feedback into the input with  $-ve$  voltage series feedback what is output  $V_o$  ?
  - If output is maintained at 30 V but second harmonic distortion is reduced to 1%, what is the input voltage ?

6

7

MVM—47052

4

(Contd.)

7. (a) Explain Barkhausen's criterion to generate oscillations. With the help of neat sketch explain working of RC phase shift oscillator.
- (b) A Hartley oscillator has  $L_1 = 2 \text{ mH}$ ,  $L_2 = 20 \mu\text{H}$  and a variable capacitor. If the frequency of oscillations is to be changed between 950 KHz and 2050 KHz then find the range of capacitance value.

7

6

OR

8. (a) Explain working of crystal oscillator with the help of neat sketch. What are its advantages over other types of filter ?
- (b) Explain working of monostable multivibrator.
9. (a) Draw the circuit and explain the working of class A push-pull amplifier with input and output transformer.
- (b) A power transistor is operating in class A is to deliver a maximum of 5 W power to a load of  $4 \Omega$ . The quiescent point is adjusted for symmetrical clipping and  $V_{cc} = 20 \text{ V}$  with ideal characteristics.
- (i) What is turn ratio  $\frac{n_2}{n_1}$  ?

7

6

7

7

MVM—47052

5

(Contd.)

12. (a) Explain how FET is used as a voltage variable resistance. 4
- (b) Draw and explain the small signal equivalent model of JFET. 6
- (c) For P-channel Si FET with  $a = 2 \times 10^{-4}$  cm and channel resistivity  $\rho = 10 \Omega$  cm, find the pinch off voltage. 3